

Multiple Output Power Supply for Audio Amplifiers

Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Audio	PKS607YN	60 W, 200 W pk	195 – 265 VAC	±26 V, -15 V, 10 V, 5 V	Flyback

Design Highlights

- Effectively replaces linear transformer-based power supplies in home audio applications
- Low component count, compact and lightweight
- Energy efficiency
 - >75% efficiency at full load (60 W)
 - <300 mW no-load power consumption at 265 VAC
 - Reduces heat sink requirements and eliminates need for separate standby supply
- Excellent transient response improves audio quality
- Dual converter approach gives excellent cross-regulation between outputs
- Integrated frequency jittering, together with a low cost EMI filter, allows for CISPR-22/EN55022B conducted EMI compliance (see Figure 2)
- Integrated safety/reliability features:
 - Accurate auto-recovering, thermal shutdown function maintains safe PCB temperatures under all conditions

- Latching shutdown protects against output short circuits and open feedback loops

Operation

The universal input power supply shown in Figure 1 has two main output supplies, +26 VDC and -26 VDC, and consists of two parallel converters, which are each 30 W (continuous) and up to 100 W (peak). Each converter uses a PeakSwitch device (PKS607YN) and shares a common input stage. The ±26 V outputs can each deliver an output current of 3.8 A peak and 1.15 A continuous. The combined power of both converters is thus 60 W (continuous) and 200 W (peak). Applications include audio amplifiers, where high peak power requirements exist for short time durations. Amplitude and duration of peak current is determined by duty cycle, thermal environment and heat-sinking.

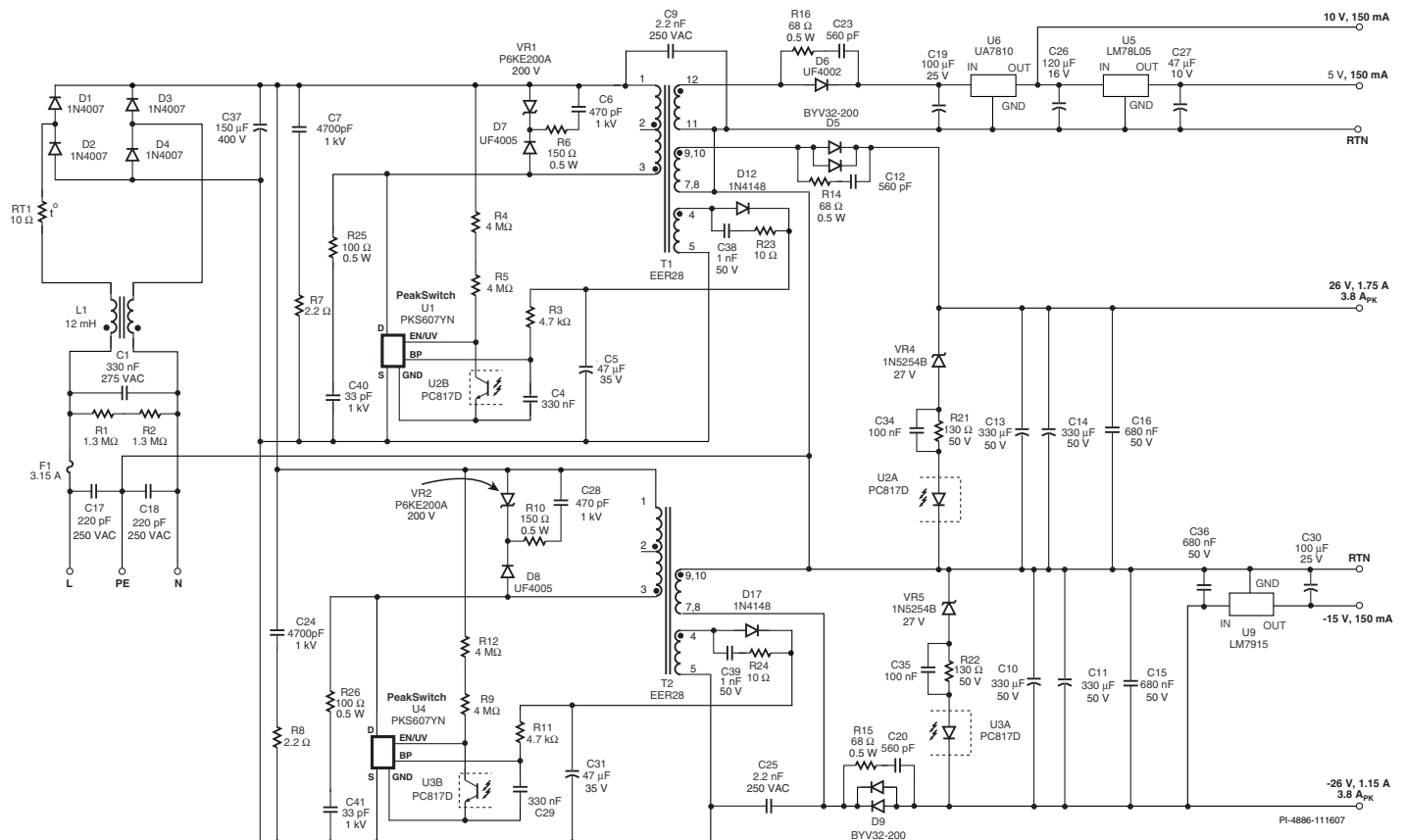


Figure 1. Schematic of a 60 W continuous and 200 W Peak Audio Amplifier Power Supply.

Common mode choke, L1, and the four Y-capacitors, C9, C17, C18 and C25, form the common mode EMI filter. Common mode choke L1 also works in conjunction with X-capacitor C1 to provide differential mode EMI filtering.

The controller in U1 (U4) skips switching cycles to regulate the output voltage based on feedback to its EN/UV pin. When the current pulled out of this pin exceeds 240 μ A, a low logic level (disable) is generated. At the beginning of each cycle, the EN/UV pin state is sampled, and if high, the power MOSFET is turned on for that cycle (enabled); otherwise the power MOSFET remains off (disabled).

During start-up, switching is inhibited until the input voltage is above the undervoltage threshold, which is determined when a current >25 μ A flows into the EN/UV pin.

Two independent feedback loops are used to control the voltages on the \pm 26 V outputs. This ensures that both outputs are tightly regulated and also ensures better cross-regulation between all outputs over line and load.

Key Design Points

- The high crest factor of the music source allows for smaller heatsinks.
- The auxiliary -15 V, 5 V and 10 V outputs are obtained from a linear regulator. To limit the power dissipation in the (5 V and 10 V) linear regulators, a second 17 V output was added to T1.
- As the value of X capacitor C1 is above 0.1 μ F, safety agency requirements specify that R1 and R2 should be used to discharge C1 such that $C1 \times (R1 + R2) \leq 1_s$.
- To reduce group pulsing of switching cycles, a high gain optocoupler U2 (U3) was used. Capacitor C34 (C35) adds high frequency gain to the feedback signal.
- In a three wire system, placing Y capacitors (C17, C18) between line/neutral and earth helps reduce common mode EMI.
- The core size and the winding wire diameter sizes (see Table 1) were chosen based on the average of the peak and the continuous output power.
- A drain to source snubber (R25, C40 and R26, C41) was added to reduce radiated EMI.

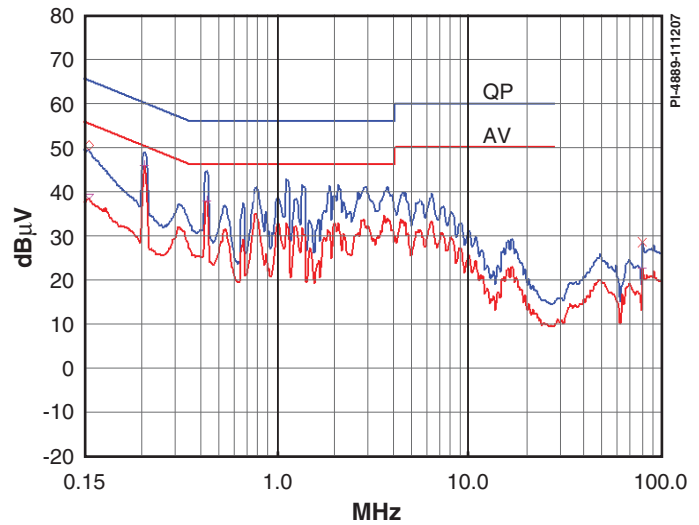


Figure 2. Conducted EMI at 230 VAC With Output Grounded (CISPR-22 Limit Lines Shown).

Transformer Parameters

Core Material	EER28 NC-2H or equivalent, gapped for ALG of 100 nH/t ²
Bobbin	EER28, 12 pin, Vertical
Winding Details	Add 3 mm margins on both sides of bobbin Primary: 18T \times 2, AWG31, tape Shield: 1T \times 1, Foil 2 mils thickness, 3 layers tape 17 V: 6T \times 2, AWG26, tape 26 V: 8T \times 4, AWG23, 3 layers tape Bias: 5T \times 2, AWG28, tape Primary: 18T \times 2, AWG31, 2 layers tape
Winding Order	Primary (3-2), Shield (NC-1), 17 V (12-11), 26 V (9,10-7,8), Bias(4-5), Primary (2-1)
Primary Inductance	129 μ H, \pm 12%
Primary Resonant Frequency	2 MHz (minimum)
Leakage Inductance	5 μ H (maximum)

Table 1. Transformer Parameters. (NC = No Connection)

Power Integrations
5245 Hellyer Avenue
San Jose, CA 95138, USA.
Main: +1 408-414-9200
Customer Service
Phone: +1-408-414-9665
Fax: +1-408-414-9765
Email: usasales@powerint.com

On the Web
www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2007, Power Integrations, Inc.